

## EST130: BASICS OF ELECTRICAL AND ELECTRONICS ENGINEERING


### MODULE 3

#### PRACTICE PROBLEMS


1. A resistor of  $50\Omega$ , an inductor of  $0.1\text{H}$  and a capacitor of  $40\mu\text{F}$  are connected in series and the combination is connected across  $220\text{V}$ ,  $50\text{ Hz}$  supply. Calculate (i) the circuit impedance (ii) resulting current (iii) power factor (iv) phase angle and (v) power consumed by the circuit.
2. Three inductive coils, each with a resistance of  $22\ \Omega$  and an inductance of  $0.05\ \text{H}$  are connected in first in star and then in delta, to a 3 phase  $415\ \text{V}$ ,  $50\ \text{Hz}$  supply. Calculate for both star and delta connections, (i) phase current and line current and (ii) total power absorbed.
3. A sinusoidal voltage  $V=230\ \angle 15^\circ$  of frequency  $50\ \text{Hz}$  is applied to a series RL circuit consisting of  $R=5\ \Omega$  and  $L=0.1\ \text{H}$ . Calculate (i) rms current and its phase angle (ii) power factor (iii) average power (iv) reactive power and (v) apparent power drawn by the circuit.
4. A balanced 3 phase load consists of 3 coils each of resistance  $6\ \Omega$  and inductive reactance of  $8\ \Omega$ . Determine the line current and power absorbed when the coils are (i) star connected (ii) delta connected across  $400\text{V}$ , 3 phase supply.
5. A resistance of  $10\Omega$ , an inductance of  $0.3\ \text{H}$  and a capacitance of  $100\mu\text{F}$  are connected in series across  $230\text{V}$ ,  $50\ \text{Hz}$  single phase supply. Calculate: i) the impedance of the circuit ii) Current through the circuit iii) Voltage across R, L and C, and iv) Power consumed by the circuit.
6. A balanced delta connected 3 phase load is fed from a 3 phase,  $400\ \text{V}$ ,  $50\ \text{Hz}$  power supply. The line current is  $20\text{A}$  and the total power absorbed by the load is  $10\text{kW}$ . Calculate (i) the impedance in each branch (ii) the power factor and (iii) the total power consumed if the same impedances are star connected.
7. When an alternating voltage of  $(80+j60)\ \text{V}$  is applied to a circuit, the resulting current flow is  $(-4+j10)\ \text{A}$ . Find the impedance, power consumed and the phase angle of the circuit.
8. Two impedances  $Z_1$  and  $Z_2$  when connected separately across a  $220\text{V}$ ,  $50\ \text{Hz}$  supply, consume  $300\text{W}$  and  $150\text{W}$  at a power factor of  $0.4$  lagging and  $0.7$  leading respectively. When the two impedances are connected in series across the same supply, find total power consumed and overall power factor.

9. A balanced three phase load has per phase impedance of  $(30+j50) \Omega$ . If the load is connected across 400V, 3 phase supply, find (i) phase current (ii) line current and (iii) power supplied to load when it is connected in (a) star (b) delta.
10. Coil A having resistance of  $20 \Omega$  and inductance of 0.2 H is connected in series with another coil B having resistance of  $15\Omega$  and inductance of 0.1H. The two coils in series are fed from 220V, 50 Hz, single phase power supply. Determine (i) the voltage across each coil (ii) power dissipated in each coil (iii) power factor of the whole circuit.
11. Three similar coils connected in star draw a total power of 1.5kW at a power factor of 0.2 lagging from a 3 phase 400V, 50Hz power supply. Calculate the resistance and inductance of each coil.
12. A series RC circuit takes a power of 7000W when connected to 200V, 50Hz supply. The voltage across the resistor is 130V. Calculate: - i) Resistance ii) Power factor iii) Current iv) Capacitance v) Impedance of the circuit.
13. A balanced star connected load of  $(8+j6) \Omega$  per phase is connected to a three phase 230V supply. Find the line current, power factor and power consumed by the load.
14. A  $50\Omega$  resistor in series with  $120\mu\text{F}$  capacitor is connected to 230V 50Hz supply. Find i) impedance ii) current iii) power factor iv) voltage across the resistor v) voltage across the capacitor.
15. A 3 phase 4 wire 400V system feeds three loads  $(10 - j8)\Omega$  each connected in star. Calculate the line currents in each phase.
16. A  $10 \Omega$  resistor and 300 mH inductor are connected in series to a 230V sinusoidal supply. The circuit current is 4A. Calculate the supply frequency and phase angle between current and voltage.
17. Three inductive coils, each with a resistance of  $22\Omega$  and an inductance of 0.05 H are connected in (i) in star and (ii) in delta, to a three phase 415 V, 50 Hz supply. Calculate for each of the above case (i) phase current and line current and (ii) total power absorbed.
18. A  $10\Omega$  resistor &  $400\mu\text{F}$  capacitor are connected in series to a 240V sinusoidal ac supply. The circuit current is 5A. Calculate the supply frequency & phase angle between current & voltage.
19. Three identical resistors of  $20\Omega$  each are connected in star to 415V, 50Hz three phase supply. Calculate (i) the total power consumed, (ii) total power consumed if they are connected in delta (iii) total power consumed, if one of the resistors is opened in both star connection and delta connections.

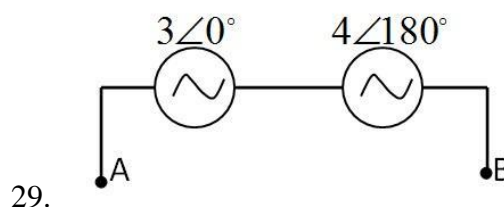20. Each phase of a delta connected load has a resistance of  $25 \Omega$  and an inductance of  $0.15 \text{ H}$ . The load is connected across a  $400 \text{ V}$ ,  $50 \text{ Hz}$ , three phase supply. Determine the line current, power factor and power consumed.
21. When a voltage of  $v = 250 \sin (314 t + \pi/3)$  is applied to a series RL circuit. The current drawn is  $i = 25 \sin (314 t + \pi/6)$ . Determine (i) power factor (ii) Active Power (iii) Impedance (iv) values of R and L.
22. A three phase star connected load consists of three identical inductive coils of resistance  $50\Omega$  and inductance  $0.3\text{H}$ . The supply voltage is  $415\text{V}$ ,  $50 \text{ Hz}$ . Calculate (i) phase current (ii) line current (iii) power factor (iv) total power consumed.
23. In a single phase ac circuit consisting of an impedance of  $10\Omega$ , the RMS value of applied voltage is  $230\text{V}$ . i) Write down the expression for instantaneous voltage, ii) If the current lags the applied voltage by  $30^\circ$  write down the expression for instantaneous current, iii) Calculate the power consumed in the circuit.
24. A resistance of  $5 \Omega$  and an inductor of  $15\text{mH}$  are connected in series across a  $230\text{V}$   $50\text{Hz}$  single phase ac supply. Calculate the (i) current (ii) power factor (iii) power consumed (iv) What value of capacitor must be connected in series with this combination to improve the power factor to  $0.9$ .
25. A balanced three phase load consists of three coils each having resistance of  $4\Omega$  and inductance  $0.02\text{H}$ . It is connected to a  $415\text{V}$ ,  $50\text{Hz}$ , 3-phase ac supply. Determine the phase voltage, phase current, power factor and active power when the loads are connected in (i) star (ii) delta.
26. Find the values of circuit elements in a two element series circuit which consumes  $700\text{W}$  at a power factor of  $0.707$  leading. The applied voltage is a single phase ac voltage given by
- $$v = 141.4 \sin (314t).$$
27. A resistance of  $120\Omega$  and capacitive reactance of  $250\Omega$  are connected in series across a single phase ac voltage source. If a current of  $0.9\text{A}$  is flowing in the circuit find (i) power factor (ii) supply voltage (iii) Active power (iv) reactive power
28. Find the total voltage across the terminals A and B of the circuit shown in Fig.




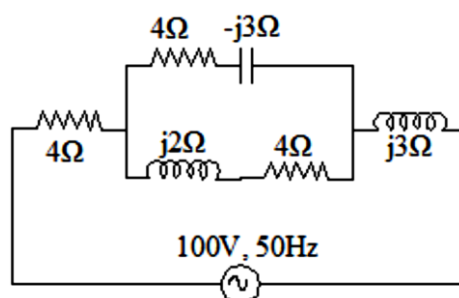30. A series circuit consisting of a capacitor of  $2 \mu\text{F}$  and a resistance of  $500 \Omega$ . An AC source is connected to the circuit which draws a current of  $50 \angle 0 \text{ mA}$ . The angular frequency of AC source is  $400\pi$ . (i) draw the circuit and find the source voltage (ii) find the voltage across the capacitor and resistor (iii) draw the voltage phasor diagram.
31. A  $220\text{V}$ ,  $50\text{Hz}$  single phase sinusoidal voltage produces a current of  $2.2\text{A}$  in a purely inductive coil. Determine (i) inductive reactance of the coil (ii) inductance (iii) power absorbed (iv) expression for applied voltage and current.
32. A capacitor and resistor are connected in series across a  $120 \text{ V}$ ,  $50 \text{ Hz}$  supply. The circuit draws a current of  $1.144 \text{ A}$ . If power loss in the circuit is  $130.8 \text{ W}$ , find the values of resistance and capacitance.
33. For an ac circuit, if  $v(t) = 160 \sin (\omega t + 10^\circ)$  and  $i(t) = 5 \sin (\omega t - 20^\circ)$ ; find the power factor and active power absorbed by the circuit. Draw the phasor diagram.
34. Two coils A and B are connected in series across a  $240 \text{ V}$ ,  $50 \text{ Hz}$  ac supply. The resistance of A is  $5 \Omega$  and the inductance of B is  $0.015 \text{ H}$ . If the input from the supply is  $3 \text{ kW}$  and  $2 \text{ kVAR}$ , find the inductance of coil A and resistance of coil B. Calculate the voltage across each coil.
35. A three phase star connected load consumes a total of  $12 \text{ kW}$  at a power factor of  $0.8$  lagging when connected to a 3 phase,  $400 \text{ V}$ ,  $50 \text{ Hz}$  power supply. Calculate the resistance and inductance of load per phase.
36. A 3 phase 4 wire star connected load of phase impedances  $Z_1 = (16 + j12) \Omega$ ,  $Z_2 = (14 - j21) \Omega$  and  $Z_3 = 25 \Omega$  is connected across a  $254 \text{ V}$ ,  $50 \text{ Hz}$  ac supply. Calculate the current in each phase of the load and power consumed by the load.
37. Calculate the real power, reactive power, apparent power and power factor of the circuit.



38. Two impedances  $(10 + j5\Omega)$  and  $(25-j10\Omega)$  are connected in parallel across 100V, 50Hz supply. Find the total current, branch currents, power factor and power consumed.
39. The apparent power drawn by an AC circuit is 10KVA and active power is 8KW. What is the reactive power and power factor of the circuit?
40. A capacitor of capacitance  $79.5 \mu\text{F}$  is connected in series with a non-inductive resistance of  $30 \Omega$  across 100 V, 50 Hz supply. Find (i) impedance (ii) current (iii) phase angle and (iv) equation for instantaneous value of current.
41. The voltage across  $150 \Omega$  resistor is  $150 \sin (2\pi \times 103t)$  V. At what value of 't' does the current through the resistor equal to -0.26 A and what is instantaneous power at this time t ?
42. A Coil of resistance  $50 \Omega$  and inductance 100 mH is connected in series with a capacitor of  $500 \mu\text{F}$  is connected across a 230 V, 50 Hz ac supply. Find (i) Current through the coil (ii) Power consumed (iii) Reactive power and (iv) Voltage across the coil. Also draw the phasor diagram with voltage as the reference vector.
43. The load to a three phase power supply consists of three similar coils connected in star. The line currents are 25A and the kVA and kW inputs are 20 and 11 respectively. Find (i) the phase and line voltages (ii) the reactive power input (iii) the resistance and reactance of each coil.
44. An R-L series circuit is supplied from an ac voltage source  $v(t) = 12 \cos 4t$  V. The complex power delivered by the source is  $S = 3.6+j7.2$  VA. Calculate the values of the resistance, R, and the inductance, L. Evaluate the power factor.
45. A three-phase four-wire system has a balanced load in Y-connection. The phase impedance of the load is  $Z_{\text{ph}} = 10\angle 30^\circ \Omega$ . If the line-to-line voltage is  $V_{\text{ll}} = 400$  V rms, evaluate the phase currents in polar form. Evaluate the total active power.
46. Two impedances,  $10\angle -30^\circ$  and  $20\angle 60^\circ$  are connected in parallel. Evaluate the equivalent impedance. What is the nature (capacitive or inductive) of the equivalent impedance? If a current of  $10\angle 45^\circ$  is passing through the parallel combination, calculate the voltage across the combination and express it in rectangular form. Evaluate the currents in each of the impedances.
47. A coil of resistance  $8\Omega$  and inductance 0.03H is connected to an a.c supply of 240V, 50Hz. Calculate: i) The current, power and power factor of the circuit. ii) The value of capacitance which when connected in series with the above coil causes no change in the value of current and power taken from the supply.

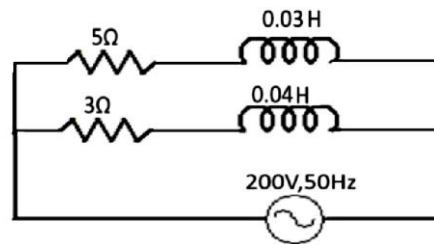48. A non-inductive resistor of  $10\Omega$  is connected in series with a choke coil having internal resistance of  $1.2\Omega$  and is fed from a  $200\text{V}$ ,  $50\text{ Hz}$  supply. Current flowing through the circuit is  $8\text{A}$ . Calculate: i) Inductance of the choke coil, ii) Voltage across the choke coil, iii) Power absorbed by the choke coil, iv) Power absorbed by non-inductive resistor v) Total power absorbed.
49. For the circuit shown in figure determine: i) The admittance in each branch, ii) Total admittance, iii) Total current drawn, iv) Circuit power factor, v) Power absorbed.



50. A balanced delta connected load consists of  $(5+j3)\Omega$  in each branch. The line voltage is  $300\sqrt{2}$  volts. Find: i) Line and phase currents, ii) Real and apparent power.
51. Two impedances  $Z_1$  and  $Z_2$  when connected separately across a  $200\text{ V}$   $50\text{ Hz}$  supply consume powers of  $100\text{ W}$  and  $60\text{ W}$  at power factors of  $0.5$  lagging and  $0.6$  leading respectively. If the impedances are now connected in series across the same supply, determine the power absorbed and resulting power factor.
52. A current of  $5\text{A}$  flows through a non inductive resistance in series with a choke coil when supplied at  $250\text{V}$ ,  $50\text{Hz}$ . If the voltage across the resistance is  $125\text{V}$  and that across the coil is  $200\text{V}$ , calculate (i) Impedance, reactance and resistance of the coil (ii) Power absorbed by the coil and (iii) Total power absorbed by the circuit.
53. A balanced delta connected load of each arm has a resistance of  $40\ \Omega$  per phase. Calculate the line, phase currents and power of the circuit if it is connected across a  $440\text{V}$ ,  $50\text{ Hz}$  supply.
54. A series connected load draws a current  $i(t) = 4 \cos (100\pi t + 10)$  A when applied across  $v(t) = 120 \cos (100\pi t - 20)$  V. Find the value of load impedance and circuit power factor.
55. A resistance  $R$ , an inductance  $L= 0.01\text{H}$  and a capacitance  $C$  are connected in series. When a voltage  $v = 400 \cos (3000t - 10)$  V is applied, the current flowing is  $10\sqrt{2} \cos (3000t - 55)$  A. Find  $R$  and  $C$ .

56. The total power consumed in a balanced star connected load is 20kW at 0.8 pf lag when supplied from a three phase 400 V, 50 Hz source. Calculate the line current, resistance and inductance of the load impedance.
57. A balanced delta connected load connected across a 440V, 50 Hz three phase supply draws a line current of 16 A which lags behind the phase voltage by an angle of  $36.86^\circ$ . Calculate the impedance of the load, phase current, power factor, and total power.
58. A non inductive resistor of  $10\Omega$  is connected in series with a choke coil having an internal resistance of  $1.2\Omega$  and is fed from a 200 V, 50 Hz supply. The current flowing through the circuit is 8 A. Calculate (i) Inductance of the choke coil (ii) Voltage across the choke coil (iii) Power absorbed by the choke coil (iv) Power absorbed by the non-inductive resistor (v) Phasor diagram of voltage.
59. A 50Hz sinusoidal voltage of  $(40+j30)$  V is applied to a series RL circuit resulting in a current of  $(4+j1)$  A. Calculate (i) Impedance of the circuit (ii) Power consumed in the circuit (ii) Power factor of the circuit.
60. A 3 phase four wire 400V, RYB system supplies a star connected load with  $Z_R=10\angle 0^\circ$ ,  $Z_Y=15\angle 30^\circ$  and  $Z_B=10\angle -30^\circ$ . Find the line currents and neutral current.